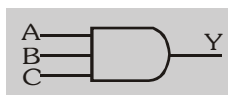


## NEET PHYSICS

### Topic - Logic Gates

1. The output of the given logic gate is 1 when inputs A, B and C are such that :-

- (1)  $A = 1, B = 0, C = 1$
- (2)  $A = 1, B = 1, C = 0$
- (3)  $A = B = C = 0$
- (4)  $A = B = C = 1$




2. The truth table given below is for :-

- (1) OR gate
- (2) AND gate
- (3) XNOR gate
- (4) XOR gate

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

3. The arrangement shown in figure performs the logic function of a/an ..... gate :-

- (1) OR
- (2) XOR
- (3) NAND
- (4) AND

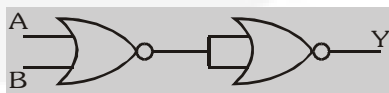



4. The output of gate is low when at least one of its input is high. This is true for :-

- (1) NOR
- (2) OR
- (3) AND
- (4) NAND

5. A two inputted XOR gate produces an output high only when its both inputs are :-

- (1) same
- (2) different
- (3) low
- (4) high

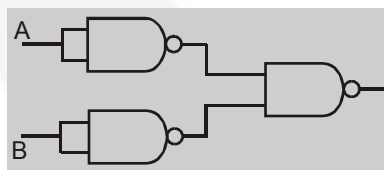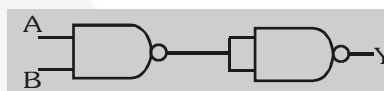6. You are given two circuits as shown in following figure. The logic operation carried out by the two circuit are respectively :-



- (1) AND, OR
- (2) OR, AND
- (3) NAND, OR
- (4) NOR, AND

7. Which of the following Boolean expression is not correct :-

- (1)  $\overline{\overline{A \cdot B}} = A + B$
- (2)  $\overline{\overline{A + B}} = A \cdot B$
- (3)  $\overline{\overline{A \cdot B}} = A \cdot B$
- (4)  $\overline{1} + \overline{1} = 1$

8. In Boolean algebra, which of the following is not equal to zero :-



- (1)  $A \cdot \overline{A}$
- (2)  $A \cdot 0$
- (3)  $\overline{A + \overline{A}}$
- (4)  $\overline{\overline{A \cdot 0}}$

9. Digital circuits can be made by repetitive use of :-  
 (1) OR gate (2) AND gate  
 (3) NOT gate (4) NAND gate

10. Which of the following relation is valid in Boolean algebra :-  
 (1)  $A + \bar{A} = 0$  (2)  $A + A = 2A$   
 (3)  $A + \bar{A} = 1$  (4)  $A + \bar{A} = A$

11. In Boolean algebra  $Y = A + B$  means that :-  
 (1) Y is the sum of A and B  
 (2) Y exists when either A or B or both A and B exist  
 (3) Y exists only when both A and B exist  
 (4) Y exists when either A or B exists but not when both A and B exist

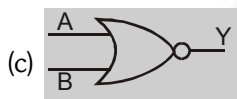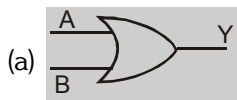12. Given below are four logic symbols. Those for OR, NOR and NAND gates are respectively :-



- (1) a, d, c (2) d, a, b  
 (3) a, c, d (4) d, b, a

13. The truth table shown below is for which of the following gates :-

- (1) XNOR  
 (2) AND  
 (3) XOR  
 (4) NOR

A	B	Y
1	1	1
0	1	0
1	0	0
0	0	1

14. When all the inputs of a NAND gate are connected together, the resulting circuit is :-  
 (1) a NOT gate (2) an AND gate  
 (3) an OR gate (4) a NOR gate

15. Which of the following pairs are universal gates :-  
 (1) NAND, NOT (2) NAND, AND  
 (3) NOR, OR (4) NAND, NOR

16. A NAND gate followed by a NOT gate is :-  
 (1) an OR gate (2) an AND gate  
 (3) a NOR gate (4) a XOR gate

17. The NOR gate is logically equivalent to an OR gate followed by :-  
 (1) an inverter (2) a NOR gate  
 (3) a NAND gate (4) All of above

18. The output of a two input NOR gate is in state 1 when :-  
 (1) either input terminals is at 0 state  
 (2) either input terminals is at 1 state  
 (3) both input terminals are at 0 state  
 (4) both input terminals are at 1 state

19. 'Output is LOW if and only if all the inputs are HIGH' Indicate the logic gate for which the above statement is true :-  
 (1) AND (2) OR  
 (3) NOR (4) NAND


20. The truth table shown is of :-

- (1) NAND gate  
 (2) NOR gate  
 (3) XOR gate  
 (4) XNOR gate

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

21. The output Y of the combination of gates shown is equal to :-

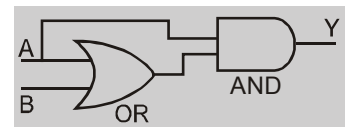
- (1) A  
 (2)  $\bar{A}$   
 (3)  $A + B$   
 (4) AB




22. Which of the following relations is valid for Boolean algebra :-  
 (1)  $A + A = A$  (2)  $A \cdot A = A$   
 (3)  $A \cdot \bar{A} = 0$  (4) all

23. What would be the output of the circuit whose Boolean expression  $Y = A\bar{B} + AB$  when  $A = 1$ ,  $B = 0$  :-  
 (1) 1  
 (2) 0  
 (3) both (1) & (2)  
 (4) none of these

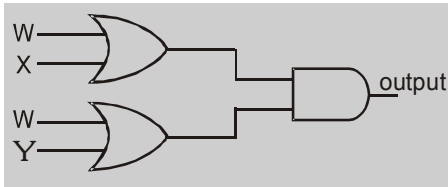
24. The diagram of a logic circuit is given below. The output of the circuit is represented by :-



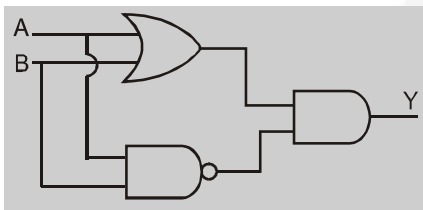- (1)  $W \cdot (X + Y)$                       (2)  $X \cdot (X \cdot Y)$   
 (3)  $W + (X + Y)$                       (4)  $W + (X \cdot Y)$
25. The following configuration of gates is equivalent to :-



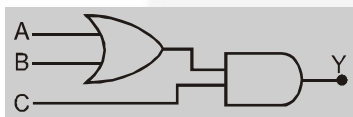
- (1) NAND    (2) OR    (3) XOR    (4) NOR
26. To get an output 1, the input ABC should be :-



- (1) 101    (2) 100    (3) 110    (4) 010

27. The output of 2 input gate is 1 only if its inputs are equal. It is true for :-  
 (1) NAND    (2) AND    (3) EX-NOR    (4) EX-OR

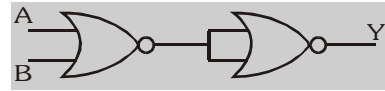
28. The circuit-shown here is logically equivalent to :-



- (1) OR gate                                      (2) AND gate  
 (3) NOT gate                                      (4) NAND gate

29. A two-input NAND gate is followed by a single-input NOR gate. This logic circuit will function as :-  
 (1) an AND gate                                      (2) an OR gate  
 (3) a NOT gate                                      (4) a NOR gate

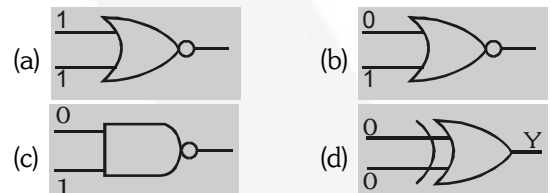30. Which of the following will have an output of 1 :-



- (1) a                      (2) c                      (3) b                      (4) d

## Answer Key

Que.	1	2	3	4	5	6	7	8	9	10
Ans.	4	3	1	1	2	1	4	4	4	3
Que.	11	12	13	14	15	16	17	18	19	20
Ans.	2	3	1	1	4	2	4	3	4	3
Que.	21	22	23	24	25	26	27	28	29	30
Ans.	1	4	1	4	3	1	3	1	1	2